


EXP-3
VLSI ENGINEERING
ANALOG
OTA

SWAGATA NASKAR
19EC30047

Aim :

To design a working two stage Operational Transconductance Amplifier(OTA) using PMOS & NMOS


Circuit Design :

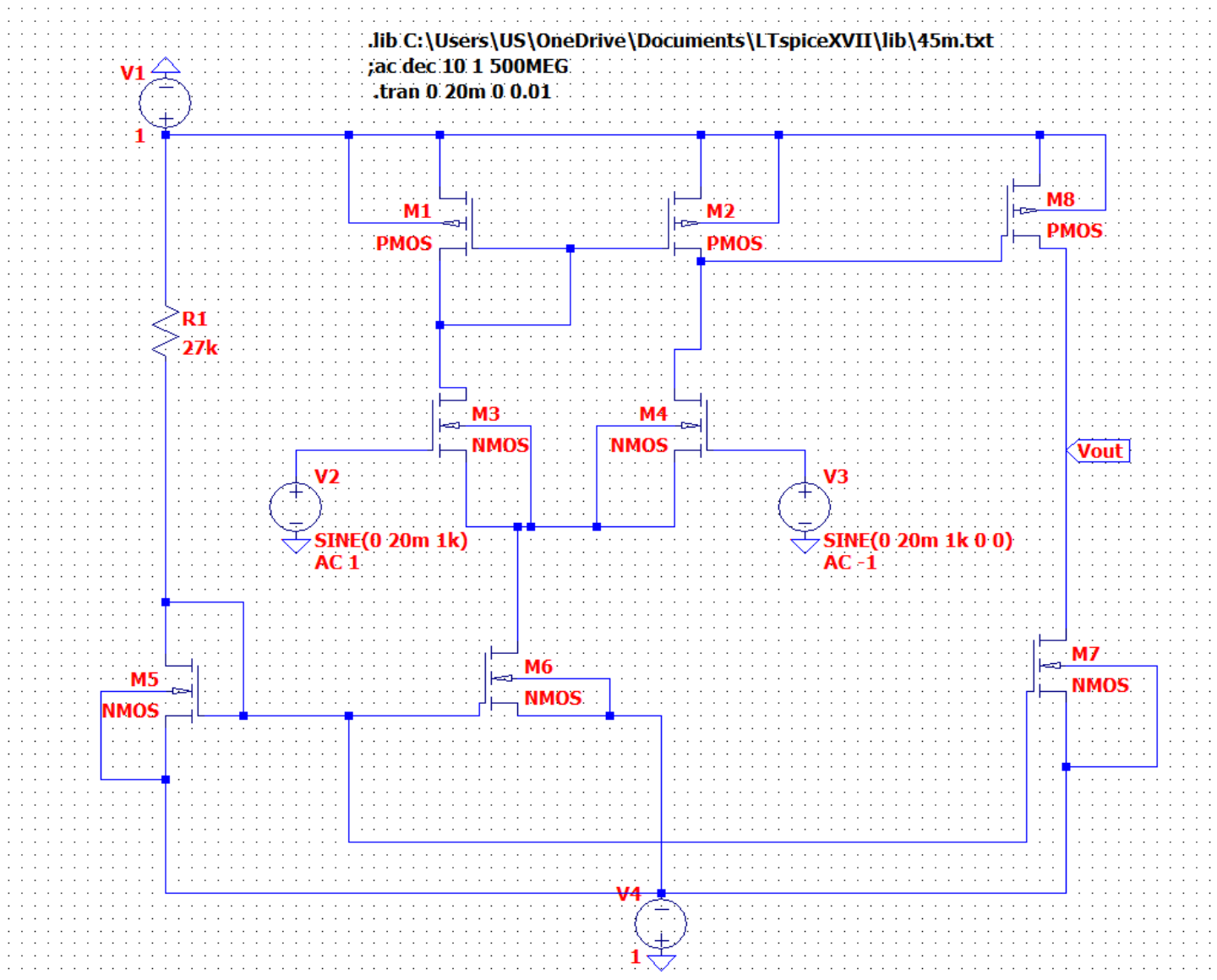


Dimensions :

M1 & M2	PMOS	L=500n	W=9u
M3 & M4	NMOS	L=500n	W=3u
M5 & M6	NMOS	L=500n	W=6u
M7	NMOS	L=500n	W=38.5u
M8	PMOS	L=500n	W=90u

Graph : Plot of Ad:

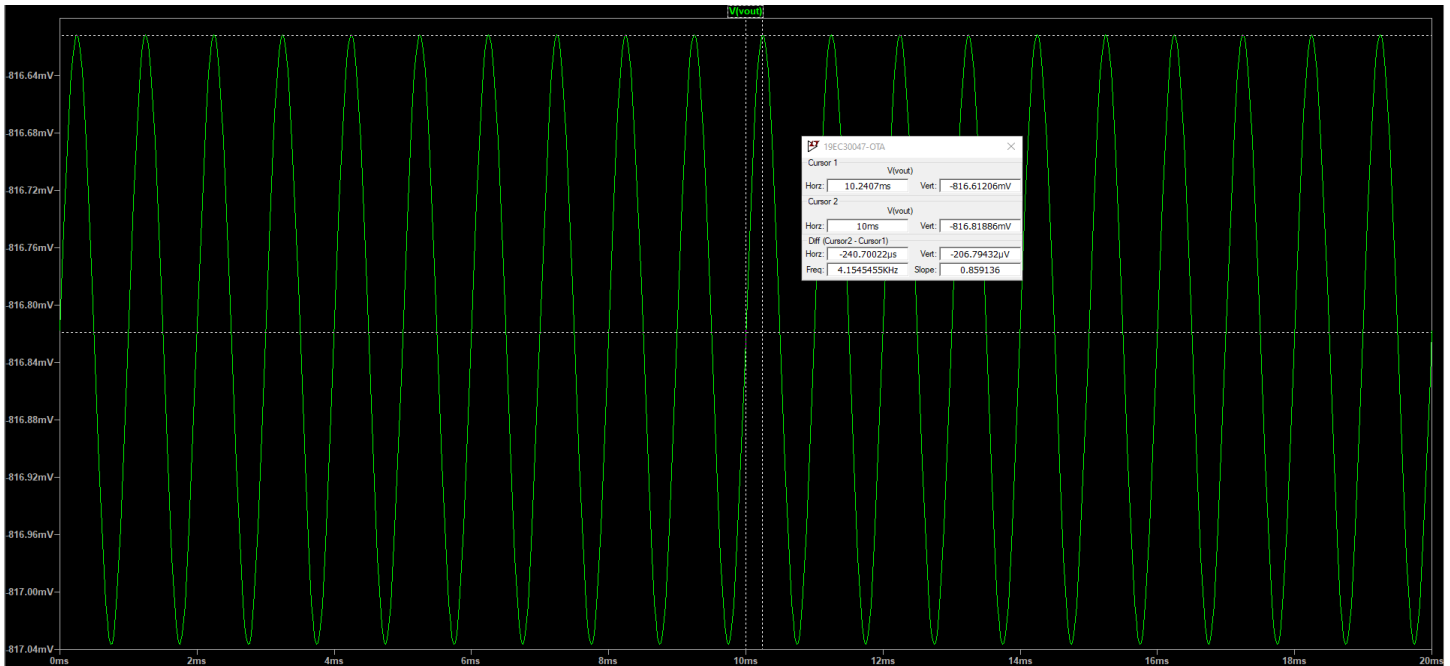

Gain Plot:

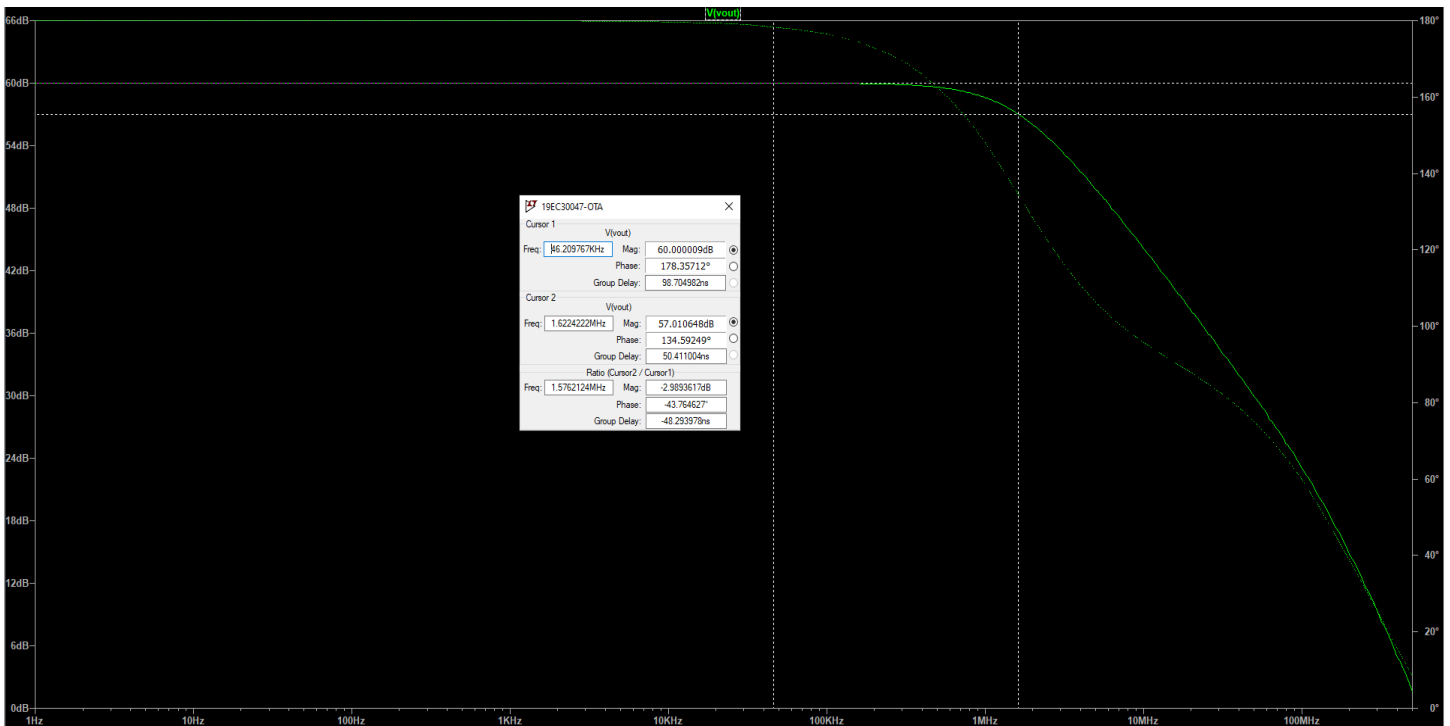

Gain = 60.000009dB

Gain bandwidth = 1.5762124MHz

Take the Value of R1 is 27k. Cause in 27k the graph shown exact value.

Our Target Values are,

Ad = 60dB

Gain Bandwidth = 1MHz.

Discussion :

- The maximum Gain Value depends on the values of M_2 & M_8 (both W/L values).
- If we increase the value of both M_7 & M_8 then we can see the gain will decrease. But if we increase the Width(w) value of the PMOS (M_7) and decrease the Width (w) value of the NMOS (M_8) then the gain value is increasing and we get a good gain value to follow this path.
- The resistance's output depends on the width and length of the transistors.
- If we increase the current through the current mirror then the amplifier's gain will be decrease.